

Figure 7-54  
T-bird tail lights.

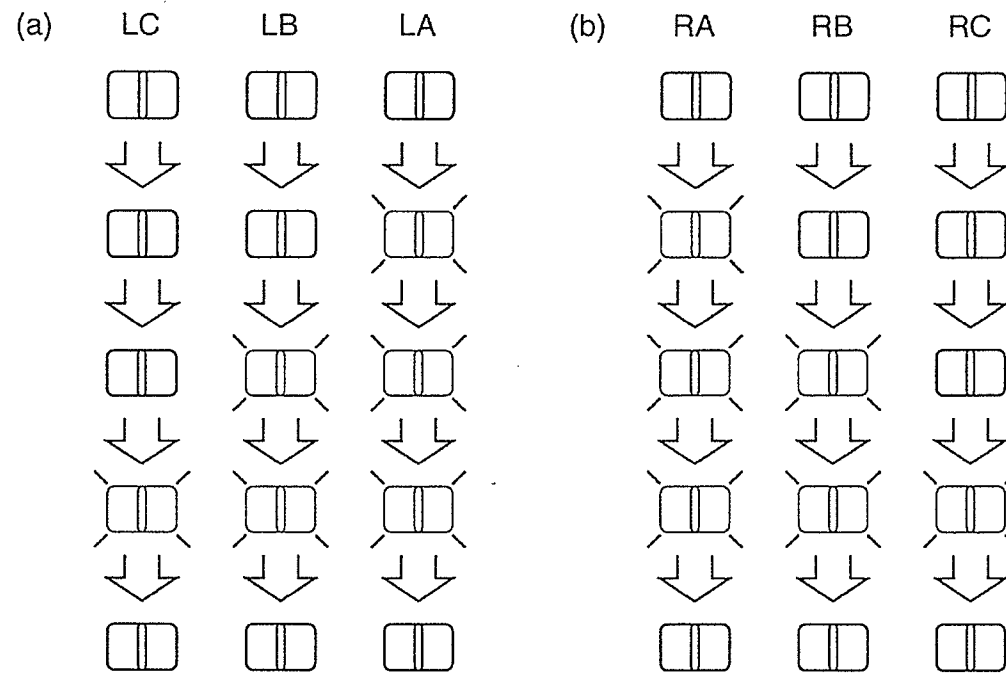


Figure 7-55

Flashing sequence for T-bird tail lights: (a) left turn; (b) right turn.

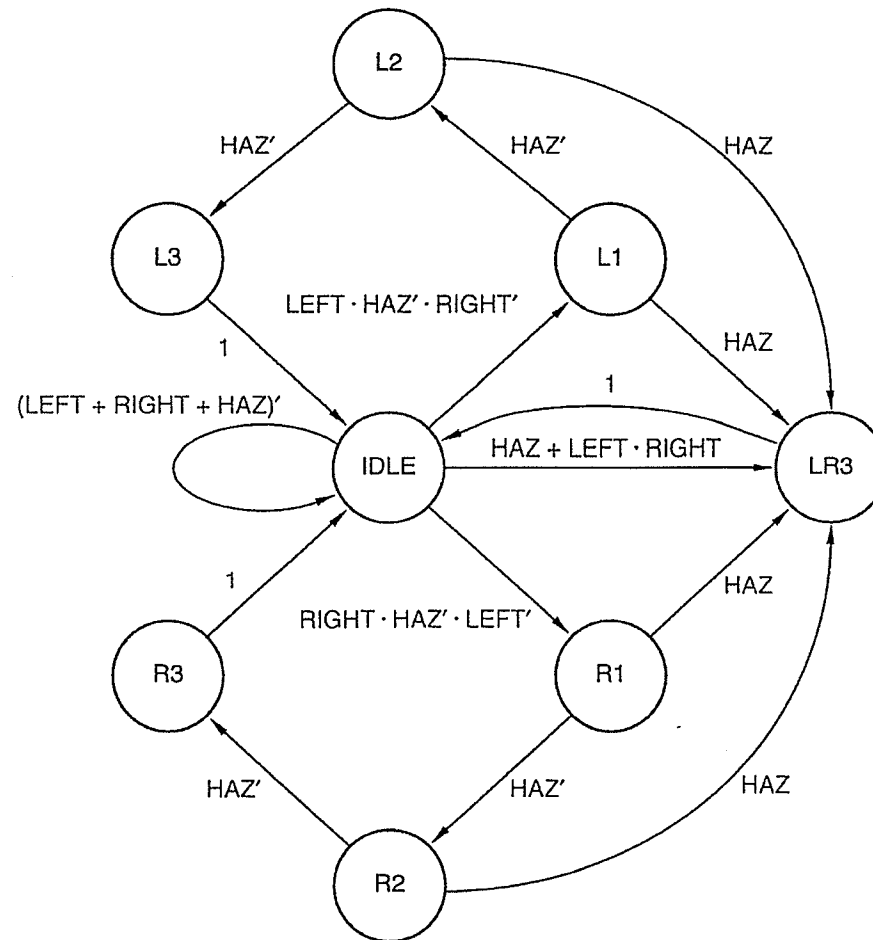


Figure 7-58  
Enhanced state diagram for T-bird tail lights.

From *Digital Design: Principles and Practices*, Fourth Edition, John F. Wakerly, ISBN 0-13-186389-4.  
©2006, Pearson Education, Inc., Upper Saddle River, NJ. All rights reserved.

Q0\*

Q1\*

Q2\*

next states

S	Q2	Q1	Q0	Transition Expression	S	Q2	Q1	Q0
IDLE	0	0	0	$(\text{LEFT} + \text{RIGHT} + \text{HAZ})'$	IDLE	0	0	0
IDLE	0	0	0	$\text{LEFT} \cdot \text{HAZ}' \cdot \text{RIGHT}'$	L1	0	0	1
IDLE	0	0	0	$\text{HAZ} + \text{LEFT} \cdot \text{RIGHT}$	LR3	1	0	0
IDLE	0	0	0	$\text{RIGHT} \cdot \text{HAZ}' \cdot \text{LEFT}'$	R1	1	0	1
L1	0	0	1	$\text{HAZ}'$	L2	0	1	1
L1	0	0	1	$\text{HAZ}$	LR3	1	0	0
L2	0	1	1	$\text{HAZ}'$	L3	0	1	0
L2	0	1	1	$\text{HAZ}$	LR3	1	0	0
L3	0	1	0	1	IDLE	0	0	0
R1	1	0	1	$\text{HAZ}'$	R2	1	1	1
R1	1	0	1	$\text{HAZ}$	LR3	1	0	0
R2	1	1	1	$\text{HAZ}'$	R3	1	1	0
R2	1	1	1	$\text{HAZ}$	LR3	1	0	0
R3	1	1	0	1	IDLE	0	0	0
LR3	1	0	0	1	IDLE	0	0	0

Table 7-14

Transition list for T-bird tail-lights state machine.

<i>State</i>	<i>Q2</i>	<i>Q1</i>	<i>Q0</i>
IDLE	0	0	0
L1	0	0	1
L2	0	1	1
L3	0	1	0
R1	1	0	1
R2	1	1	1
R3	1	1	0
LR3	1	0	0

Table 7-13

State assignment for T-bird tail-lights state machine.